

Using Switches

We use electrical machines to do work for us at home. They heat water, wash clothes, clean dishes, and suck dust off the floor. We turn them on and off with a **switch**.

On and Off

When a switch is on, it completes the circuit and an electric current flows. When a switch is off, it makes a gap in the circuit. The electric current stops flowing.

