## Unit 9 Vocabulary part 2- Chapter 35 pg. 713

- 1. circuit
- 2. in series
- 3. in parallel
- 4. series circuit
- 5. parallel circuit
- 6. schematic diagram

